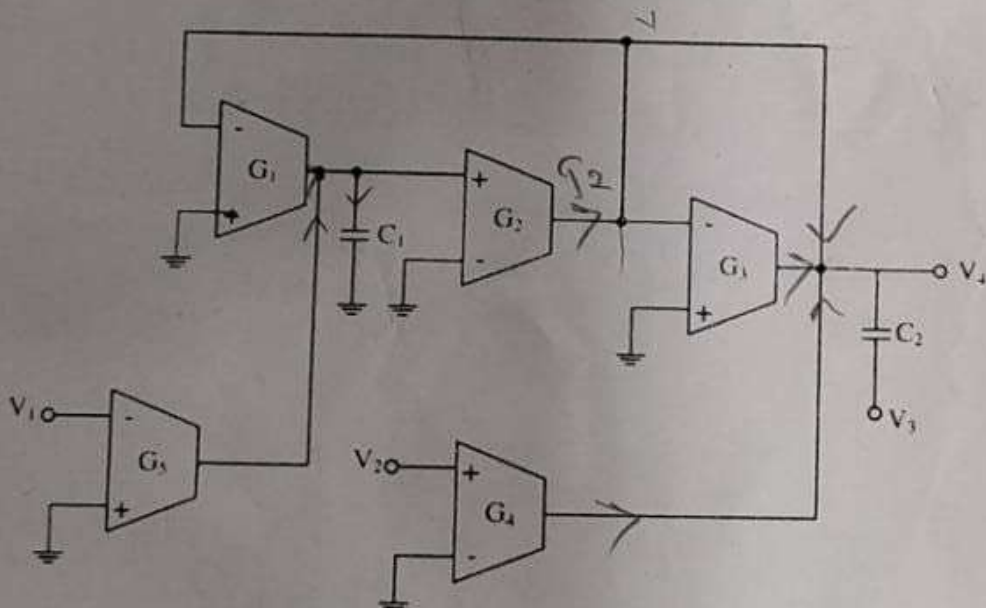


Time: 1 Hour

Note: Attempts all questions

Questions	Marks	
<p>1.</p> <p>Sketch a neat circuit diagram of floating inductor using Op-amps and passive components and hence, derive the expression of the value of inductance realized.</p>	8	
<p>2.</p> <p>Derive the expression of <math>V_4</math> in terms of <math>V_1</math>, <math>V_2</math> and <math>V_3</math> in Fig. 1 and show that the circuit behaves like a MISO-type biquad and also calculate the value of cut-off frequency when <math>C_1 = C_2 = 0.01\mu F</math>, <math>V_{cc} = \pm 15V</math>, <math>R_b</math> of <math>100K\Omega</math> connected between pin no 5 and ground of each OTAs.</p>  <p>Fig. 1</p>	8	<p><math>P_0 = 1</math></p> <p>gr</p> <p><math>\textcircled{G_2} + \textcircled{G_1}</math></p> <p>VBE</p>